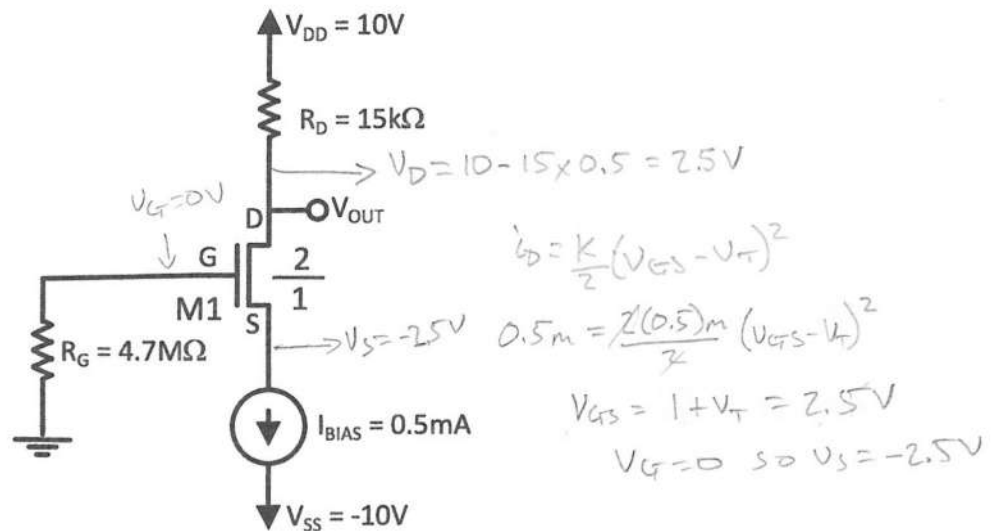



15pts  
1) The circuit below is biased using a constant current source to set  $I_{DS}$  for the MOSFET.  $V_T = 1.5V$  and  $K_n' = 0.5mA/V^2$ , and remember  $K_n = (W/L) K_n'$ .

- Find all of the DC node voltages:  $V_D$ ,  $V_S$ ,  $V_G$ , and  $V_{GS}$ .
- What is the maximum swing at the drain for which the MOSFET remains in saturation (without taking into account the signal swing at the gate)?



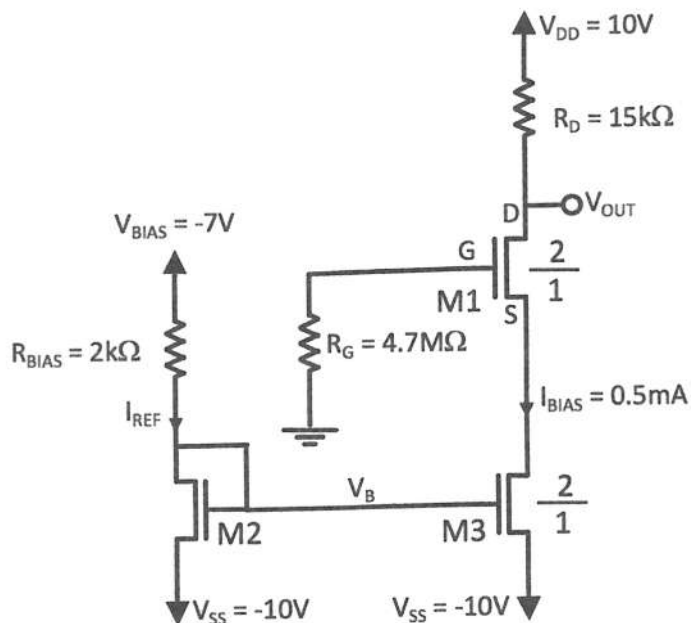2) Now complete the design of the current mirror in the circuit below to provide the bias current of 0.5mA for the circuit of problem 1.

- What is the voltage at  $V_B$ , and what is  $V_{GS}$  for M2 and M3?
- What is  $W/L$  for M2?



$$\begin{aligned}
 I_{REF} &= \frac{-V_{BIAS} - V_B}{R_{BIAS}} \\
 &= \frac{-7 - (-7.5)}{2k} \\
 &= \frac{0.5}{2k} = 0.25 \text{ mA}
 \end{aligned}$$


For M2

$$\begin{aligned}
 i_D &= \frac{K}{2} (V_{GS} - V_T)^2 \\
 0.25 &= \frac{K}{2} (2.5 - 1.5)^2 \\
 K &= 0.5 \Rightarrow \boxed{\frac{W}{L} = 1}
 \end{aligned}$$

For M3

$$\begin{aligned}
 i_D &= \frac{K}{2} (V_{GS} - V_T)^2 \\
 0.5 \text{ mA} &= \frac{2(0.5)K}{2} (V_{GS} - V_T)^2 \\
 V_{GS} &= 1 + V_T = 2.5 \text{ V} \\
 \text{So } \boxed{V_B = -7.5 \text{ V}} \\
 \boxed{V_{GS} = 2.5 \text{ V}}
 \end{aligned}$$

This page left blank to continue problem 3.  
comparing your answers to part (e) and part (f).

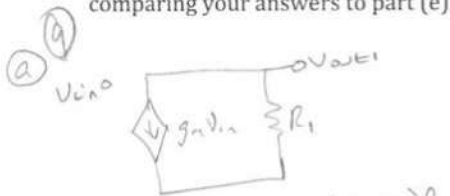(a) 

$$\frac{v_{out1}}{v_{in}} = -g_m R_1 = -k (V_{GS} - V_t) R_1$$


$$= -4(1.6 - 1) = -2.4$$

$G_1 = -2.4$

(b)  $G_1 = -g_m R_1 // R_{LOAD}$

$$= -4(1.6 - 1) \cdot 0.66$$

$G_1 = -1.6$

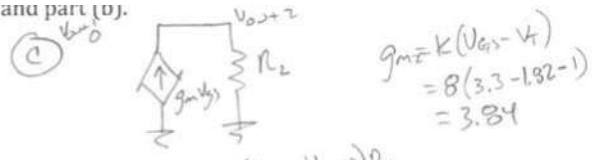(c) 

$$g_{m2} = k(V_{GS} - V_t)$$

$$= 8(3.3 - 1.92 - 1)$$

$$= 3.84$$

$$v_{out2} = g_{m2}(v_{in2} - v_{out2})R_2$$

$$v_{out2}(1 + g_{m2}R_2) = g_{m2}v_{in2}R_2$$

$$\frac{v_{out2}}{v_{in2}} = \frac{g_{m2}R_2}{1 + g_{m2}R_2} = \frac{1}{1 + 1/g_{m2}R_2}$$

$$G_2 = \frac{1}{1 + 1/7.68} = 0.88$$

(d)  $G_2 = \frac{1}{1 + 1/g_{m2}(R_2 // R_{LOAD})}$

$$= \frac{1}{1 + 1/3.84} = 0.79$$

(e)  $G_{12} = G_1 \times G_2$

$$= -2.4 \times 0.79$$


$$= -1.9$$

(f) The overall gain of the 2 stage amp is higher when driving  $R_{LOAD}^{(1.9k)}$  compared to if the first common source stage directly drives  $R_{LOAD}^{(1.6k)}$  which shows the second stage is functioning as a voltage buffer.

(g)  $g_{m1}$  and  $g_{m2}$  correspond to the operating point from problem #2.

$$V_T = 1V$$

$$K_n' = 2 \text{ mA/V}^2$$

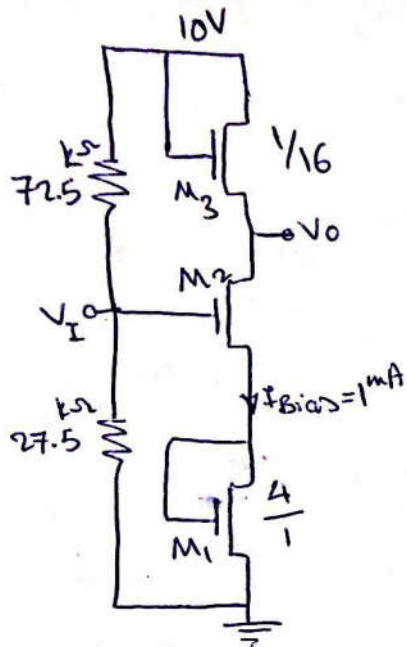

Note: For  $M_1$  &  $M_3$ , because their Gate and Drain are Connected, they will be in Saturation region because:

$$V_{GD} = 0, \text{ Saturation Conditions } \begin{cases} V_{GS} > V_T \\ V_{DS} > V_{GS} - V_T \\ \Rightarrow V_{GD} < V_T \end{cases}$$

$$\Rightarrow 0 < 1V$$

$$a) V_I = \frac{27.5^{k\Omega}}{27.5^{k\Omega} + 72.5^{k\Omega}} \times 10^V = 2.75^V$$

$$\text{Thevenin equivalent: } R_{th} = \frac{27.5^{k\Omega} \times 72.5^{k\Omega}}{27.5^{k\Omega} + 72.5^{k\Omega}} \approx 20^{k\Omega}$$

For  $M_3$ :

$$i_D = \frac{K}{2} (V_{GS3} - V_T)^2$$

$$1^{mA} = \frac{2^{mA/V^2}}{16 \times 2} (V_{GS3} - 1)^2$$

$$\Rightarrow V_{GS3} = 4 + 1 = 5^V \Rightarrow (10 - V_O) = 5^V$$

$$\Rightarrow \boxed{V_O = 5^V}$$

For  $M_1$ :

$$i_D = \frac{K}{2} (V_{GS1} - V_T)^2$$

$$1^{mA} = \frac{4(2^{mA/V^2})}{2} (V_{GS1} - 1)^2$$

$$1/4 = (V_{GS1} - 1)^2$$

$$V_{GS1} = 1/2 + 1 = 1.5^V$$

$$\Rightarrow (V_{G1} - 0) = 1.5^V \Rightarrow \boxed{V_{G1} = 1.5^V}$$

$$\text{For } M_2: V_{GS2} = V_S - V_{G1} = 2.75 - 1.5 = 1.25^V$$

$$V_{DS} = V_O - V_{G1} = 5 - 1.5 = 3.5 > 0.25^V$$

$M_2$  is in saturation:


$$i_D = K/2 (V_{GS} - V_T)^2$$

$$1^{mA} = K/2 (1.25 - 1)^2 = K/2 (1/4)^2$$


$$K = 32 = \frac{W}{L} (2^{mA/V^2})$$

$$\Rightarrow \boxed{W/L = \frac{16}{1}}$$

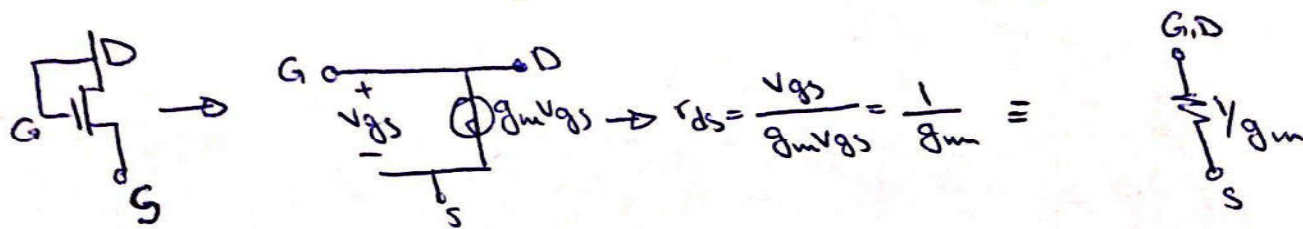b) First draw the small signal model for  $M_1$  and  $M_3$ :



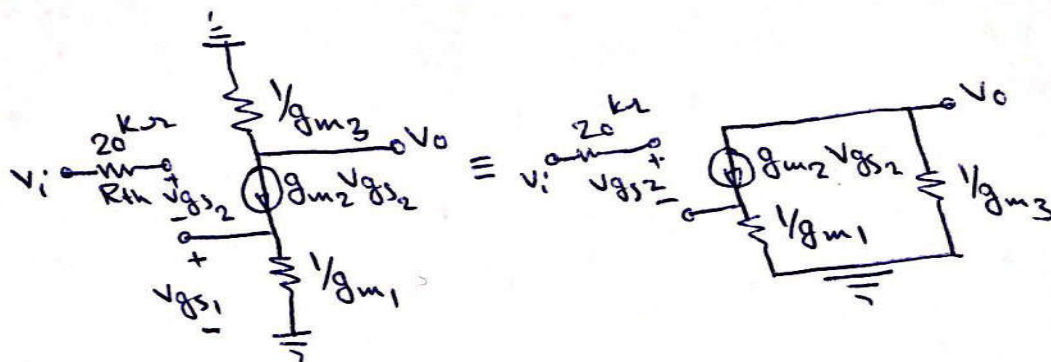now use this model in the circuit's small signal model:



$$V_i = V_{gs2} + V_{gs1}, \quad g_{m2}V_{gs2} = g_{m1}V_{gs1} \Rightarrow V_{gs1} = \frac{g_{m2}}{g_{m1}} V_{gs2}$$

$$\Rightarrow V_i = V_{gs2} + \frac{g_{m2}}{g_{m1}} V_{gs2} = \left(1 + \frac{g_{m2}}{g_{m1}}\right) V_{gs2} = \frac{g_{m1} + g_{m2}}{g_{m1}} V_{gs2}$$

$$\Rightarrow V_o = -g_{m2}V_{gs2} \times \frac{1}{g_{m3}} = -\frac{g_{m2}}{g_{m3}} \times \frac{g_{m1}}{g_{m1} + g_{m2}} V_i$$

$$g_m = \frac{2I_D}{V_{GS} - V_T} = K(V_{GS} - V_T) \Rightarrow \begin{cases} g_{m1} = K_1(V_{GS1} - V_T) = 4 \times 2^m (1.5 - 1) = 4^{mS} \\ g_{m2} = K_2(V_{GS2} - V_T) = 16 \times 2^m (1.25 - 1) = 8^{mS} \\ g_{m3} = K_3(V_{GS3} - V_T) = \frac{1}{16} \times 2^m (5 - 1) = 0.5^{mS} \end{cases}$$

$$\Rightarrow V_o = -\frac{8^m}{0.5^m} \times \frac{4^m}{4^m + 8^m} V_i \approx -5.3 V_i$$

$$\Rightarrow \boxed{\frac{V_o}{V_i} \approx -5.3}$$

$$\boxed{\frac{V_o}{V_i} = -\frac{g_{m2}}{g_{m3}} \frac{g_{m1}}{g_{m1} + g_{m2}} V_i}$$

$$\boxed{\frac{V_o}{V_i} = -\frac{K_2(V_{GS2} - V_T)}{K_3(V_{GS3} - V_T)} \times \frac{K_1(V_{GS1} - V_T)}{K_2(V_{GS2} - V_T) + K_1(V_{GS1} - V_T)} V_i}$$