

SELECTING S.S. OPERATING POINT



$$A = -g_m R_L$$

$$= -K(V_{IN} - V_T) R_L$$

$$V_{DD} = 10V, K = 1mA/V^2, R_L = 10K\Omega, V_T = 1V$$

Find V_{IN} for $|A| = 12$

$$12 = 1 \times (V_{IN} - 1) 10K$$


$$V_{IN} = 2.2V$$

What is maximum V_{PP} for V_{IN}

From Chap 7

$$-1 + \frac{\sqrt{1 + 2V_{DD} R_L K}}{R_L K} + V_T \geq V_{IN} \geq V_T$$


$$2.32V \geq V_{IN} \geq 1$$

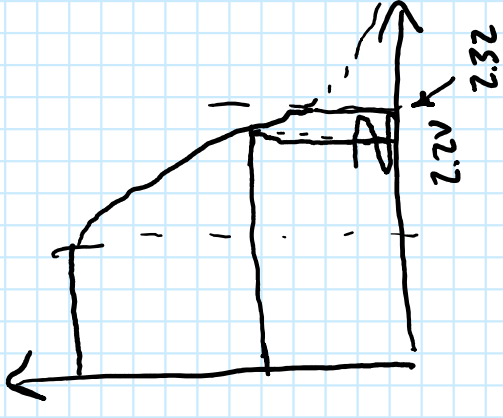

$$\text{max } P-P = (2.32 - 2.2) \times 2$$

$$= 0.24V_{PP}$$

TWO-STAGE AMP

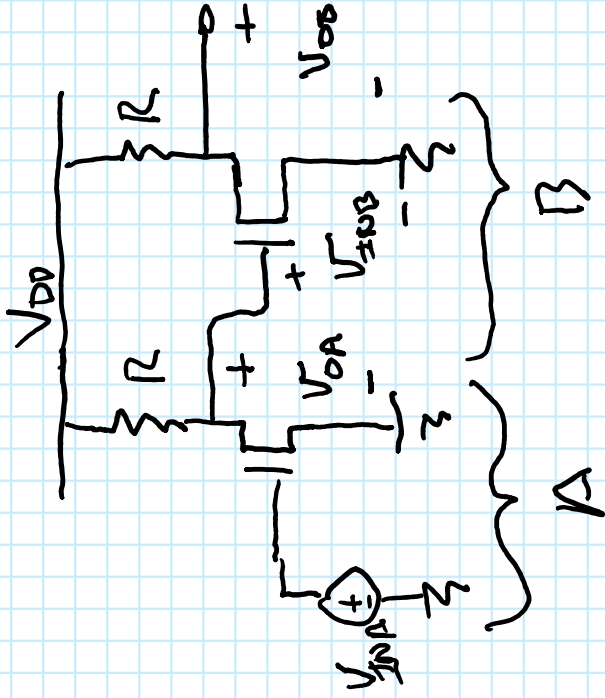

$$\frac{V_{OB}}{V_{INA}} = \frac{V_{OA}}{V_{INA}} \times \frac{V_{OB}}{V_{INB}}$$

$$V_{INA} = 2.2V$$


$$V_{OA} = V_{DD} - I_{DA}R$$

$$= V_{DD} - \frac{K}{2} (V_{INA} - V_T)^2 R$$

$$= 10 - \frac{1}{2} (2.2 - 1)^2 10$$

$$= 2.8V > 2.32V \rightarrow \text{NOT A VALID OPERATING POINT FOR B}$$

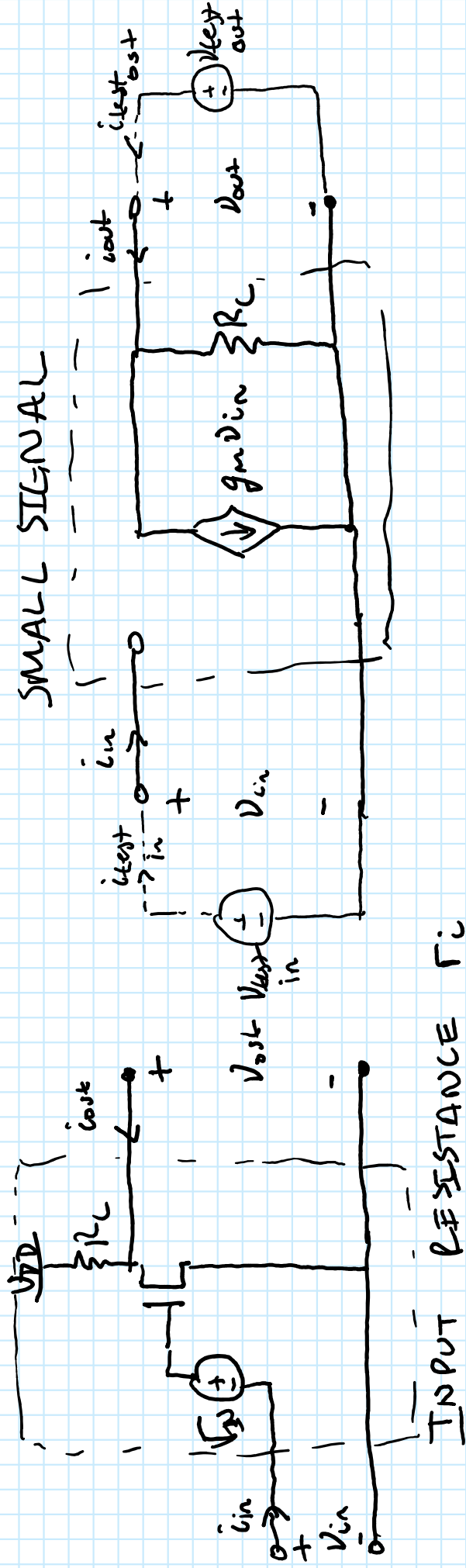INPUT & OUTPUT RESISTANCE, CURRENT AND POWER GAIN



— Change in input current for a small change in input voltage

① apply small v_{test} , measure i_{test}


② all other independent voltage sources are shorted
current sources are opened

$$r_{in} = \frac{v_{test, in}}{i_{test, in}} \Rightarrow \infty$$

$$r_{out} = \frac{v_{test, out}}{i_{test, out}} = R_L \Rightarrow \text{MOSFET behaves like open circuit } i_d = 0$$

CURRENT GAIN

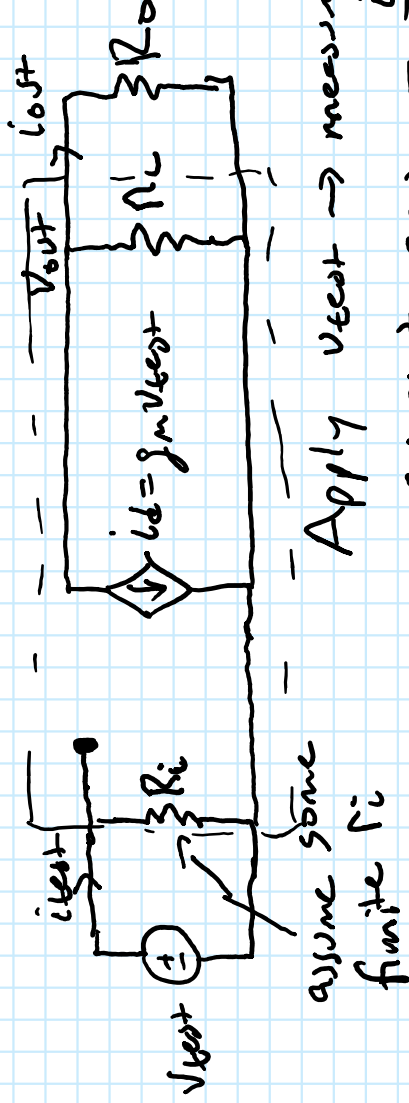Incremental change in output current
 incremental change in input current



Apply $v_{test} \rightarrow$ measure i_{test} & i_{out}

$$\text{Current gain} = \frac{i_{out}}{i_{test}}$$

$$i_{out} = \frac{v_{out}}{R_o}$$

$$i_{test} = \frac{v_{test}}{R_i}$$

$$\text{ratio} = \frac{v_{out}}{v_{test}} \cdot \frac{R_i}{R_o}$$

voltage gain

lower gain with external R_o

$$\frac{v_{out}}{v_{test}} = - \frac{g_m v_{test} (R_o \parallel R_i)}{v_{test}} = -g_m (R_o \parallel R_i)$$

if $R_i = \infty$ (MOSFET) \rightarrow C.G. $\rightarrow \infty$

$$\text{Current gain} = -g_m (R_o \parallel R_i) \frac{R_i}{R_o}$$

FOR A GIVEN
 LOAD RESISTANCE

POWER GAIN

POWER GAIN \Rightarrow ratio of

power supplied to an external load
power supplied by input source

USE SAME CIRCUIT AS CURRENT GAIN (R_i, R_o)

$$\text{Power Gain} = \underbrace{\left(\frac{V_{out} I_{out}}{V_{test} I_{test}} \right)}_{\substack{\text{Voltage gain} \\ \text{current gain}}} = \frac{P_{out}}{P_{in}}$$


$$= -g_m (R_L \parallel R_o) \cdot \left[-g_m (R_L \parallel R_o) \frac{R_i}{R_o} \right]$$

$$= g_m^2 (R_L \parallel R_o)^2 \frac{R_i}{R_o}$$

$$\text{if } R_i = \infty$$

$R_G = \infty \Rightarrow$ doesn't matter if R_i is finite


COMMON DRAIN AMP (AKA SOURCE FOLLOWER)

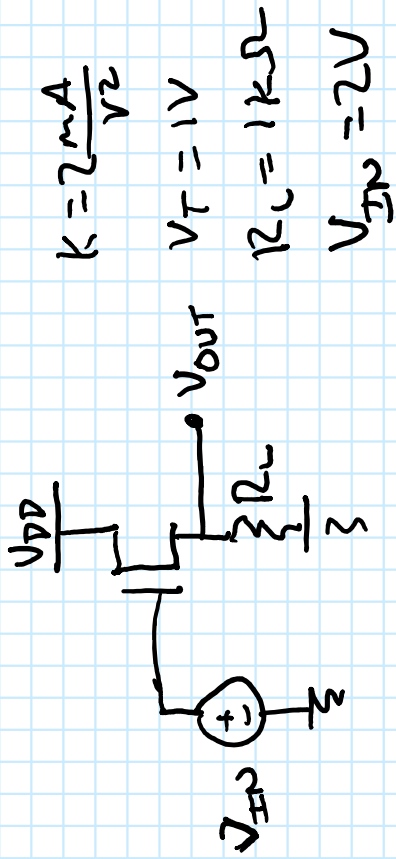

$V_{OUT} = 2.6$ or $0.4V$
 CHECK NOT cutoff
 $V_{GS} > V_T$
 $V_{IN} - V_{OUT} > V_T$

$$V_{OUT} = 0.4V$$
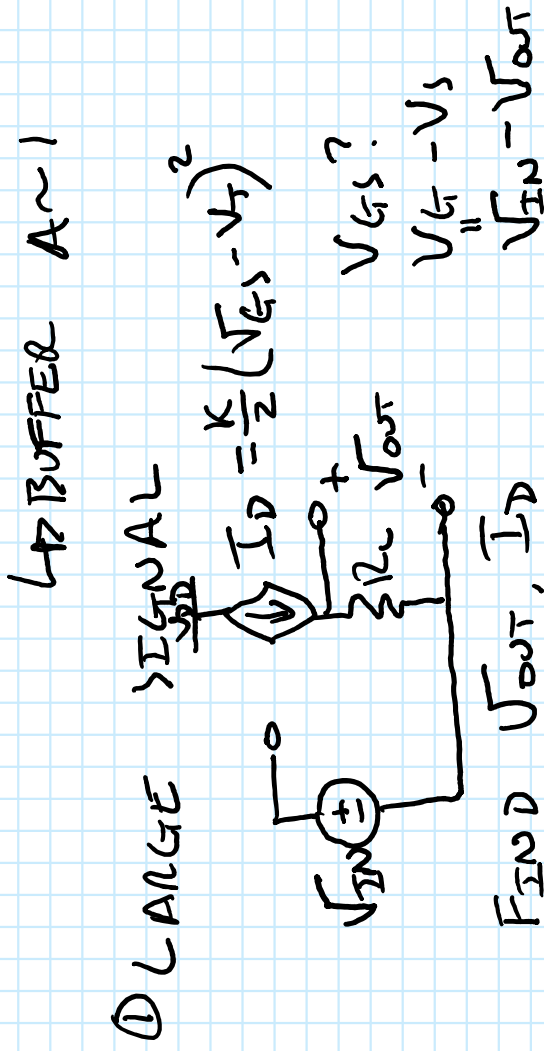
$$I_D = \frac{V_{OUT}}{R_L} = \frac{0.4}{1k\Omega} = 0.4mA$$



$$V_{OUT} = \frac{K}{2} (V_{GS} - V_T)^2 R_L$$

$$= \frac{K}{2} (V_{IN} - V_{OUT} - V_T)^2 R_L$$

$$= \frac{2}{2} (2V - V_{OUT} - 1)^2 1k$$

$$V_{OUT} = (1 - V_{OUT})^2$$

$$V_{OUT} = 1 - 2V_{OUT} + V_{OUT}^2$$

$$V_{OUT}^2 - 3V_{OUT} + 1 = 0$$

$$V_{OUT} = \frac{3 \pm \sqrt{9 - 4}}{2} = \frac{3 \pm 2.23}{2}$$