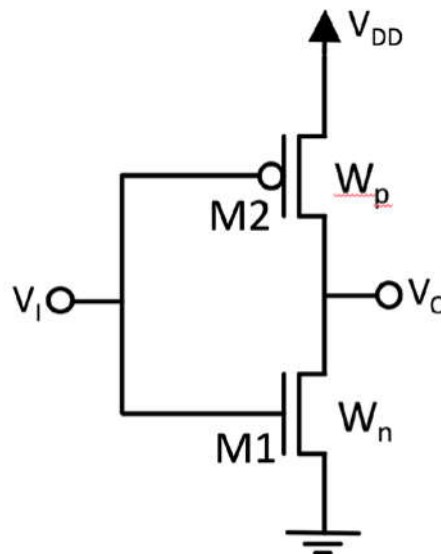


UNIVERSITY OF CALIFORNIA, SANTA BARBARA
Department of Electrical and Computer Engineering

Homework 1 – due January 18, 2018 by 5:00pm

NOTE: For all the problems here, and from now on, we'll use the common terminology for **K**. Namely, we'll use $K_n = K_n'$ (W/L) for n-MOSFETs and $K_p = K_p'$ (W/L) for p-MOSFETs. $K_n' = \mu_n C_{ox}$ and $K_p' = \mu_p C_{ox}$.

1) For the CMOS inverter circuit shown below, assume the following: $K_n' = K_p'$, $L_n = L_p = 1\mu\text{m}$, and $|V_{TP}| = V_{TN} = V_T$. Let's define the threshold as the point ($v_I = V_{TH}$) in the v_O versus v_I transfer curve where $v_O = V_{DD}/2$.



- Sketch the inverter transfer curve and mark the V_{TH} point.
- Find an expression for the inverter threshold voltage V_{TH} in terms of V_{DD} , V_T , W_n and W_p .
- If $W_n = W_p$, what is V_{TH} ? In what mode of operation are M1 and M2 when $V_I = V_{TH}$?

- d) Now assume $V_{DD} = 5V$. Fill in V_{TH} in the tables below for the cases when $V_T = 0V$ and when $V_T = 1V$.


$$V_T = 0V$$

$W_p \backslash W_n$	1	4	16
1			
4			
16			

$$V_T = 1V$$


$W_p \backslash W_n$	1	4	16
1			
4			
16			

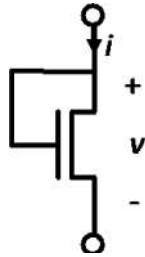2. The configuration shown below, an n-MOSFET with its drain and gate terminals connected together, is called a **diode-connected MOSFET**.




- In what mode does the MOSFET operate and why?
- Find the i - v characteristics of the two-terminal device in terms of the MOSFET parameters K and V_T .
- Plot the i - v characteristics if $K = 1\text{mA/V}^2$ and $V_T = 1\text{V}$ over the range of $v = 0$ to 5V (1V increments in voltage are sufficient)

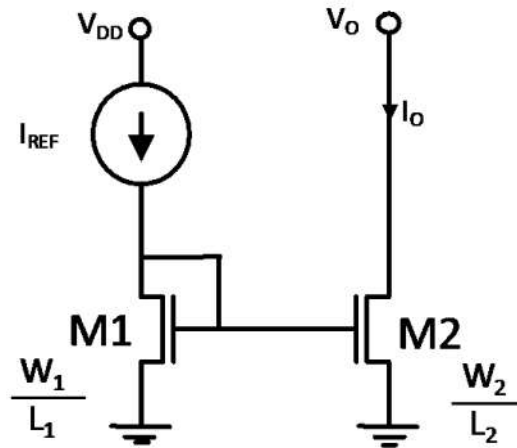3. Consider the circuit shown below. Assume that both of the transistors are matched, meaning: 1) K_n is the same for both devices M1 and M2, and is equal to 1mA/V^2 ; 2) $V_T = 0.5\text{V}$ for both M1 and M2. Recall that $K = K_n' (W/L)$, where W is the length and L is the width of the MOSFET. Further assume that $V_{DD} = 3\text{V}$ and V_O is large enough that M2 operates in the saturation regime.



- In what mode does M1 operate and why?
- Find the relationship between I_O and I_{REF} in terms of the MOSFET parameters.
- Find V_{GS} if $I_{REF} = 10\text{mA}$, $W_1 = 10\mu\text{m}$, and $L_1 = 1\mu\text{m}$.
- Find I_O under the conditions in part (c) if $W_2 = 20\mu\text{m}$ and $L_2 = 1\mu\text{m}$.
- What is the minimum value for V_O to ensure M2 is in saturation under the conditions of part (d)?

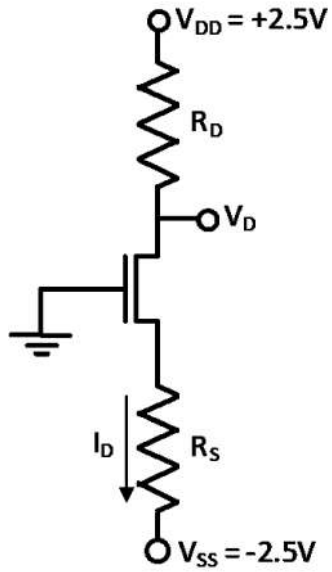4. Determine the Values of R_D and R_S such that the circuit below operates at $I_D = 0.4 \text{ mA}$ and $V_D = +0.5\text{V}$. Assume $V_T = 0.7\text{V}$, $K_n = 100\mu\text{A/V}^2$, $L = 1 \text{ }\mu\text{m}$, and $W = 32 \text{ }\mu\text{m}$.



5. Determine V_O in the circuit below in terms of the power supply voltages and MOSFET parameters (W_1, L_1, W_2, L_2, V_T). You can assume that K_n is the same for both of the n-MOSFETs and that both M1 and M2 are biased in the saturation region.

