
Homework 1 Solution 10 B

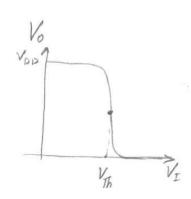

$$|I_{SD}|_{P} = |I_{DS}|_{N}$$

$$K_{p} = K_{p}'(\frac{W_{p}}{L_{p}})$$
 $K_{n} = K_{n}'(\frac{W_{n}}{L_{n}})$
 $V_{TN} = |V_{Tp}| = V_{T}$

$$V_{Th} = \sqrt{\frac{\omega_{p}}{\omega_{n}}} \left(V_{DD}\right) + V_{T}\left(1 - \sqrt{\frac{\omega_{p}}{\omega_{n}}}\right)$$

$$1 + \sqrt{\frac{\omega_{p}}{\omega_{n}}}$$

VI	=	0
0		

Wp	11	4	16
1	2.5	5/3	1
4	10/3	2.5	
16	4		2.5

	V_T	-= 1	
WAW	1	4	16
/	2.5	2	1.6
4	3	2.5	
16	3.4		2.5


problem #2

a)
$$V_G = V_D$$

 $V_{DS} > V_{GS} - V_T \longrightarrow Saturation$

b)
$$i = \frac{K}{2} (V_{G5} - V_{T})^{2}$$

$$i = \frac{K}{2} (V_{G5} - V_{T})^{2}$$

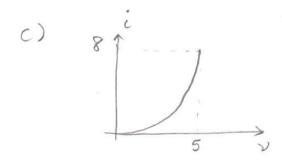

Problem # 3

a) For M,
$$V_D = V_G \rightarrow V_{DS} > V_{GS} - V_T \rightarrow Saturation$$

b)
$$Inf = \frac{K_1}{2} (V_{GS_1} - V_T)^2$$
 $I_0 = \frac{K_2}{2} (V_{GS_2} - V_T)^2$
 $V_{GS_1} = V_{GS_2}$

$$\frac{I_o}{I_{nf}} = \frac{\left(\frac{W_2/L_2}{L_2}\right)}{\left(\frac{W_1/L_1}{L_1}\right)}$$

$$(2) \quad |0| = \frac{10}{2} \left(V_{G5}, -0.5 \right)^{2}$$

$$V_{G5} = 1.914 V$$

d)
$$I_0 = I_{nf} \frac{(w_2/l_2)}{(w_1/l_2)} = 10 \times (2\%) = 20 \text{ mA}$$

(e)
$$V_{GS_2} = V_{GS_1} = 1.914 V$$

 $V_0 > V_{GS_2} - V_T$
 $V_0 > 1.414 V$ $V_{omin} = 1.414 V$

Problem #4

$$V_{5} = -1.2V$$
 $V_{5} - V_{55} = I_{D}R_{5}$
 $V_{5} = -0.2V \rightarrow v_{4}$
 $R_{5} = 3.25 \kappa_{1}$

$$V_D = 0.5V$$

$$V_{DD} - V_D = I_D R_D$$

$$R_{D} = \frac{V_{00} - V_{0}}{I_{D}} = 5 K_{A}$$

Problem # 5

$$\frac{k_n}{2} (V_2 - V_0 - V_T)^2 = \frac{k_n}{2} (V_1 - V_T)^2$$

$$\sqrt{\frac{\omega_2}{L_2}} \left(V_2 - V_0 - V_T \right) = \sqrt{\frac{\omega_1}{L_1}} \left(V_1 - V_T \right)$$

$$V_0 = \frac{(V_2 - V_T)\sqrt{\frac{\omega_2}{L_2}} - (V_1 - V_T)\sqrt{\frac{\omega_1}{L_1}}}{\sqrt{\frac{\omega_2}{L_2}}}$$