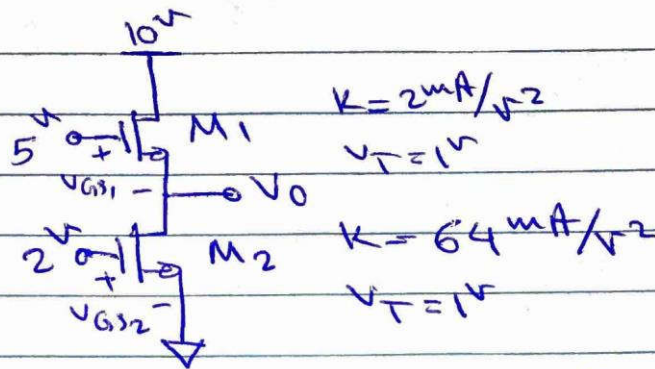


HW #3 Solutions

1. a)



$M_1 = \text{Sat} \because i_{D1} = \frac{k_1}{2} (V_{GS1} - V_{T1})^2$

$M_2 = \text{Sat} \because i_{D2} = \frac{k_2}{2} (V_{GS2} - V_{T2})^2$

$i_{D1} = i_{D2} \because \frac{k_1}{2} (V_{GS1} - V_{T1})^2 = \frac{k_2}{2} (V_{GS2} - V_{T2})^2$

$\frac{2}{2} ((5 - V_0) - 1)^2 = \frac{64}{2} ((2 - 0) - 1)^2$

$(5 - V_0 - 1)^2 = 32 (1)^2 \rightarrow V_0^2 + 16 - 8V_0 = 32$

$\rightarrow V_0^2 - 8V_0 - 16 = 0 \quad \left\{ \begin{array}{l} V_{01} = -1.657 \text{ V} \\ V_{02} = 9.657 \text{ V} \end{array} \right.$

* Checking which V_0 is valid :

$M_1 \& M_2 \text{ in Saturation} \quad \left\{ \begin{array}{l} V_{GS1} \geq V_{T1} \& V_{DS1} \geq V_{GS1} - V_{T1} \\ V_{GS2} \geq V_{T2} \& V_{DS2} \geq V_{GS2} - V_{T2} \end{array} \right.$

$\rightarrow \left\{ \begin{array}{l} 5 - V_{01} = 6.657 \text{ V} > 1 \text{ V} \quad \checkmark \\ 5 - V_{02} = -4.657 \text{ V} < 1 \text{ V} \quad \times \end{array} \right\} V_{GS1} \geq V_{T1}$

$2 - 0 = 2 \geq 1 \quad \checkmark \quad V_{GS2} \geq V_{T2}$

$\rightarrow \left\{ \begin{array}{l} V_{DS1} = 10 - V_{01} = 11.657 \text{ V} > 5.657 \text{ V} \quad \checkmark \text{ Saturation} \end{array} \right.$

5

$M_1 = \text{triode} \therefore i_{D1} = K_1 \left[(V_{GS1} - V_{T1}) V_{DS1} - \frac{V_{DS1}^2}{2} \right]$

$M_2 = \text{triode} \therefore i_{D2} = K_2 \left[(V_{GS2} - V_{T2}) V_{DS2} - \frac{V_{DS2}^2}{2} \right]$

$i_{D1} = i_{D2} \therefore K_1 \left[(V_{GS1} - V_{T1}) V_{DS1} - \frac{V_{DS1}^2}{2} \right]$

$= K_2 \left[(V_{GS2} - V_{T2}) V_{DS2} - \frac{V_{DS2}^2}{2} \right]$

$\rightarrow 2^{\mu A} \left[(5 - V_o - 1)(10 - V_o) - \frac{(10 - V_o)^2}{2} \right]$

$= 64^{\mu A} \left[(2 - V_o - 1)(V_o - 0) - \frac{(V_o - 0)^2}{2} \right]$

$\rightarrow (4 - V_o)(10 - V_o) - \frac{(10 - V_o)^2}{2} = 32 \left[V_o - \frac{V_o^2}{2} \right]$

$(10 - V_o) \left(4 - V_o - 5 + \frac{V_o}{2} \right) = 32 \left(V_o - \frac{V_o^2}{2} \right)$

$-10 - 5V_o + V_o + \frac{V_o^2}{2} = 32V_o - 16V_o^2$

$\rightarrow 33V_o^2 - 72V_o - 20 = 0 \quad \begin{cases} V_{o1} = 0.24 \\ V_{o2} = +2.43 \end{cases}$

$M_1 \& M_2 \text{ in Triode } \begin{cases} V_{GS1} > V_{T1} \& V_{DS1} < V_{GS1} - V_{T1} \\ V_{GS2} > V_{T2} \& V_{DS2} < V_{GS2} - V_{T2} \end{cases}$

$\rightarrow \begin{cases} 5 - V_{o1} = 5.24 > V_{T1} = 1 \checkmark \\ 5 - V_{o2} = 2.57 > V_{T1} = 1 \checkmark \end{cases}$

$2 - 0 = 2 > 1 \checkmark$

$V_{DS1} = 10 - V_{o1} = 10.24 > 4.24 \times \checkmark$

$V_{DS1} = 10 - V_{o2} = 7.57 > 1.57 \times \text{Saturation}$

$V_{DS2} = V_{o1} = 0.24 < 1 \times \checkmark$

This is not valid.

c) $M_1 = \text{Triode} \therefore i_{D1} = k_1 \left[(V_{GS1} - V_{T1}) V_{DS1} - \frac{V_{DS1}^2}{2} \right]$

$M_2 = \text{Saturation} \therefore i_{D2} = \frac{k_2}{2} (V_{GS2} - V_{T2})^2$

$i_{D1} = i_{D2} \therefore 2^{\mu} \left[(5 - V_0 - 1)(10 - V_0) - \frac{(10 - V_0)^2}{2} \right]$

$= \frac{64^{\mu}}{2} (2 - 1)^2$

$\Rightarrow (4 - V_0)(10 - V_0) - \frac{(10 - V_0)^2}{2} = 16$

$\Rightarrow \{ V_{01} = -4.25^V$


$V_{02} = 12.25^V$

| | |
|-----------------------------|--|
| $M_1 \text{ in Triode}$ | $\left\{ \begin{array}{l} V_{GS1} > V_{T1} \text{ \& } V_{DS1} < V_{GS1} - V_{T1} \end{array} \right.$ |
| $\&$ | |
| $M_2 \text{ in Saturation}$ | $\left\{ \begin{array}{l} V_{GS2} > V_{T2} \text{ \& } V_{DS2} > V_{GS2} - V_{T2} \end{array} \right.$ |

$\Rightarrow \left\{ \begin{array}{l} 5 - V_{01} = 9.25 > 1 \checkmark \rightarrow 10 - V_{01} = 14.25 > 8.25 \times \text{ Saturat} \\ 5 - V_{02} = -7.25 < 1 \times \\ 2 > 1 \checkmark \rightarrow V_{01} = 4.25 < 1 \times \end{array} \right.$

\Rightarrow This is not valid.

2.

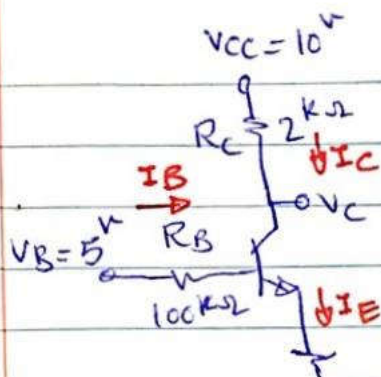

$$V_{BE} = 0.6V \rightarrow I_B = \frac{V_B - V_{BE}}{R_B} = \frac{5 - 0.6}{100k}$$

$$\rightarrow I_B = 44 \mu A$$

$$I_C = \beta I_B = 100 \times 44 \mu A = 4.4 \text{ mA}$$


$$I_C = (1 + \beta) I_B = 4.444 \text{ mA}$$

$$V_C = V_{CC} - 2^k I_C = 10 - 2^k \times 4.4 \text{ mA} = 1.2V > 0.2V \rightarrow \text{Active}$$

$$a. \beta_{\text{new}} = 112 \rightarrow I_B = 44 \mu A, I_C = 112 \times 44 \mu A = 4.928 \text{ mA}$$

$$V_C = 10 - 2^k I_C = 0.144V < 0.2V \rightarrow \text{Saturation}$$

3.

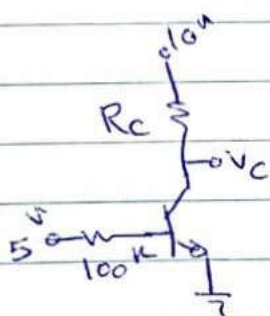

$$I_B = 44 \mu A, 50 \leq \beta \leq 150, V_{CE} \geq 0.2V$$

$$\beta_{\text{min}} = 50: I_C = \beta_{\text{min}} I_B = 50 \times 44 \mu A = 2.2 \text{ mA}$$

$$V_C = 10 - 2.2 \text{ mA} \times R_C \geq 0.2V \rightarrow R_C \leq 4.45 \text{ k}\Omega$$

$$\beta_{\text{max}} = 150: I_C = 150 \times 44 \mu A = 6.6 \text{ mA}$$

$$V_C = 10 - 6.6 \text{ mA} \times R_C \geq 0.2V \rightarrow R_C \leq 1.48 \text{ k}\Omega$$


$$\Rightarrow \boxed{R_C \leq 1.48 \text{ k}\Omega}$$

You can pick a value in this range. $R_C = 1 \text{ k}\Omega$ is a good choice.


$$a. \beta_{\text{min}} = 50: V_C = 10 - 2.2 \text{ mA} \times 1^k = 7.8V \Rightarrow 3.4V \leq V_C \leq 7.8V$$

$$\beta_{\text{max}} = 150: V_C = 10 - 6.6 \text{ mA} \times 1^k = 3.4V$$

4) Small-signal model for the BJT:

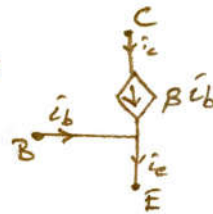

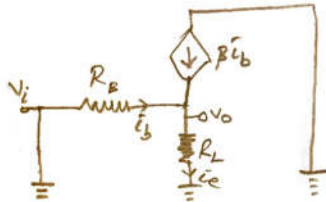Small signal model for the common-collector amplifier:



$$\hat{i}_b = (V_{in} - V_o) / R_B$$

$$\hat{i}_e = \hat{i}_b + \beta \hat{i}_b$$

$$\hat{i}_e = \frac{V_o}{R_L}$$

$$\frac{V_o}{R_L} = (\beta + 1) \hat{i}_b = (\beta + 1) \frac{V_{in} - V_{out}}{R_B}$$


$$R_B V_o = R_L (\beta + 1) (V_{in} - V_{out})$$

$$(R_L (\beta + 1) + R_B) V_o = R_L (\beta + 1) V_i$$

$$\frac{V_o}{V_i} = \frac{R_L (\beta + 1)}{R_L (\beta + 1) + R_B} = \frac{\frac{R_L}{R_B} (\beta + 1)}{\frac{R_L}{R_B} (\beta + 1) + 1}$$

$$A = \frac{V_o}{V_{in}} \approx 1 \quad \text{when} \quad \frac{R_L}{R_B} (\beta + 1) \gg 1$$

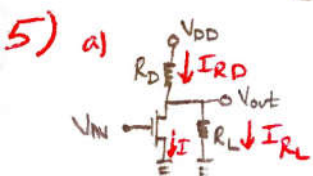In this circuit base terminal of the transistor serves as the input and the emitter is the output. When $A \approx 1$ the output voltage "follows" the input voltage. In this case the emitter voltage follows the base voltage, hence the circuit is called an emitter follower.



$$\text{Saturation: } I = \frac{K_N}{2} (V_{GS} - V_{TN})^2$$

$$I_{RD} = I + I_{RL}$$


$$\rightarrow \frac{V_{DD} - V_{out}}{R_D} = \frac{K_N}{2} (V_{GS} - V_{TN})^2 + \frac{V_{out}}{R_L}$$

$$V_{GS} = V_{IN} : V_{out} \left(\frac{1}{R_L} + \frac{1}{R_D} \right) = \frac{V_{DD}}{R_D} - \frac{K_N}{2} (V_{IN} - V_{TN})^2$$

$$V_{out} = \frac{R_L R_D}{R_L + R_D} \left(\frac{V_{DD}}{R_D} - \frac{K_N}{2} (V_{IN} - V_{TN})^2 \right)$$

$$\rightarrow V_{out} \left(\frac{R_L + R_D}{R_D R_L} \right) = -g_m V_{gs}, \quad V_{gs} = V_{in}$$
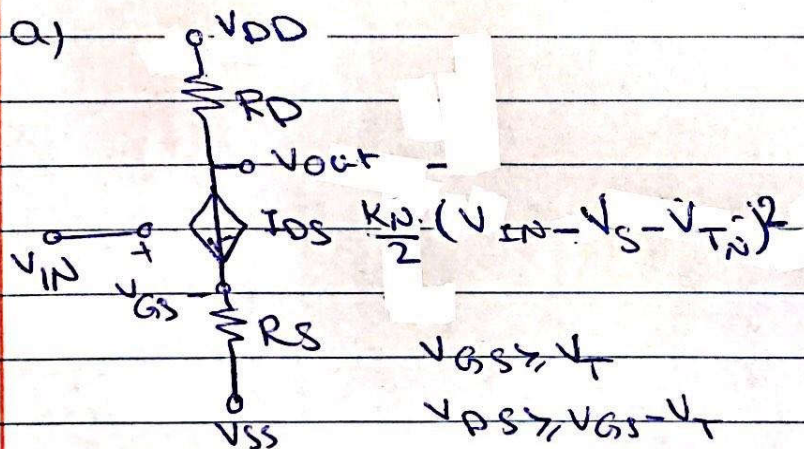
$$g_m = \frac{2 I_D}{\frac{V_{GS} - V_T}{V_{IN}}} = K_N (V_{IN} - V_T)$$



$$V_{GS} = V_{IN} - V_{SS} - R_S I_D$$

$$\Rightarrow \sqrt{I_D} = \pm \sqrt{\frac{K_N}{2}} (V_{IN} - V_{SS} - R_S I_D - V_{TN})$$

$$\left(1 + \sqrt{\frac{K_N}{2}}\right) R_{S1} I_D + \sqrt{I_D} + \sqrt{\frac{K_N}{2}} (V_{SS} + V_{TP} - V_{IN}) = 0$$

$$I_D = \frac{-2ab \pm \sqrt{1 - 4ab} + 1}{2a^2}$$


$$\Rightarrow I_D = \frac{K_N R_S (V_{SS} + V_{TN} - V_{IN}) \pm \sqrt{1 + 2K_N R_S (V_{SS} + V_{TN} - V_{IN})} + 1}{K_N R_S^2}$$

Valid

$$V_{out} = V_{DD} - R_D I_D$$

$$C_0 \left. V_{out} \right|_{V_{IN}=0} = V_{DD} - R_D \left(\frac{K_N R_S (V_{SS} + V_{TN}) - \sqrt{1 + 2K_N R_S (V_{SS} + V_{TN})} + 1}{K_N R_S^2} \right)$$


d.

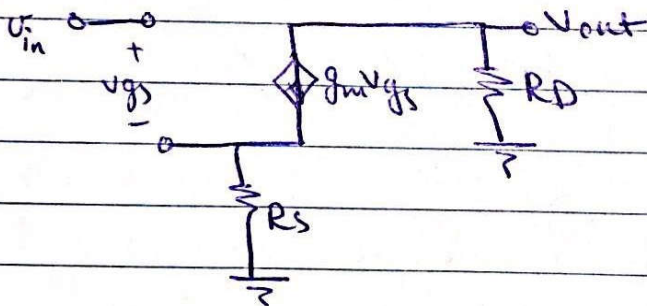

$$e. V_{out} = -R_D g_m V_{gs}, \quad V_{gs} = V_{in} - g_m R_S V_{gs} \Rightarrow V_{gs} = \frac{V_{in}}{1 + g_m R_S}$$

$$V_{out} = -R_D g_m \frac{V_{in}}{1 + g_m R_S} \Rightarrow A = \frac{V_{out}}{V_{in}} = -R_D \frac{g_m}{1 + g_m R_S}$$

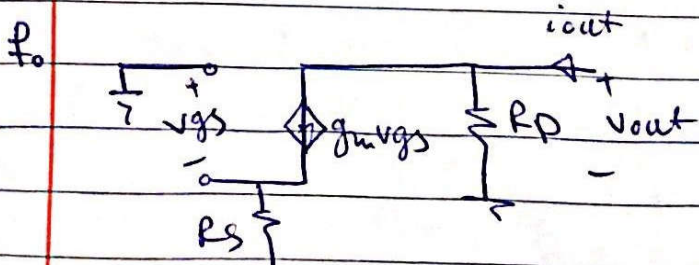
$$g_m = \frac{2I_D}{V_{GS} - V_T} = K_N (V_{GS} - V_T)$$



$$V_{gs} = -g_m R_S V_{gs} \Rightarrow V_{gs} = 0$$

$$g_m V_{gs} = 0$$
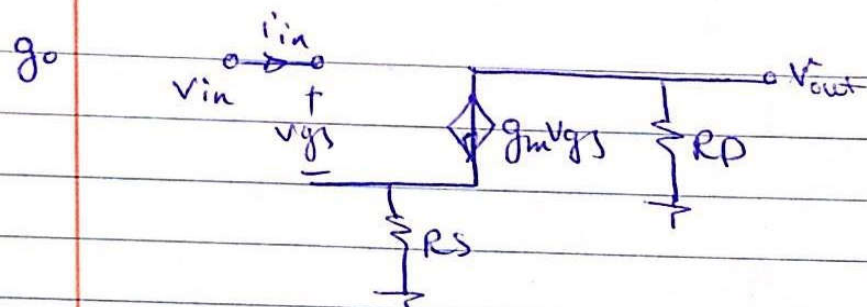
$$R_D i_{out} = V_{out} \Rightarrow i_{out} = \frac{V_{out}}{R_D}$$



$$i_{in} = 0 \Rightarrow \frac{v_{in}}{i_{in}} = \infty \Rightarrow \boxed{R_{in} = \infty}$$