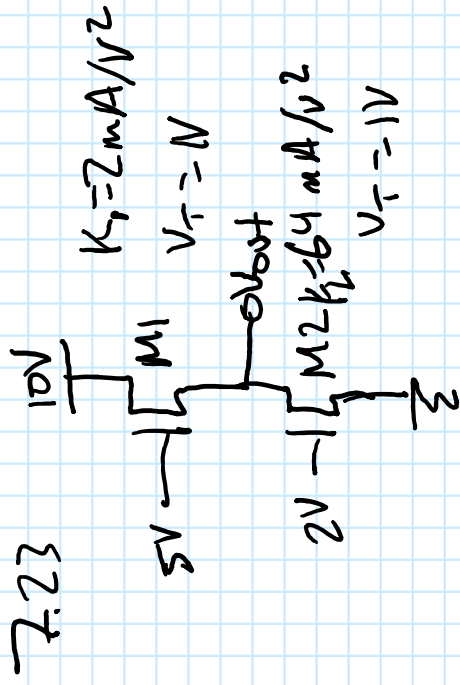


HW3 problem 1



Check M1 SAT

$$V_{DS1} \geq V_{GS1} - V_T$$

$$10 - 1.94 \geq 5 - 1.94 - 1 \checkmark$$

Check M2 triode

$$V_{DS2} < V_{GS2} - V_T$$

$$1.94 < 2 - 1 \checkmark$$

$$0.26 < 1 \checkmark$$

M1 in SAT
M2 in triode

$$\frac{K_1}{2} (V_{GS1} - V_T)^2 = K_2 \left[(V_{GS2} - V_T) V_{DS2} - \frac{V_{DS2}^2}{2} \right]$$





$$\frac{2}{2} (5 - V_{out})^2 = 64 \left[(2 - 1) V_{out} - \frac{V_{out}^2}{2} \right]$$

$$16 - 8 V_{out} + V_{out}^2 = 64 V_{out} - 32 V_{out}^2$$

$$33 V_{out}^2 - 72 V_{out} + 16 = 0$$

$$V_{out} = 0.26 \text{ or } 1.94$$

BJT ACTIVE MODEL

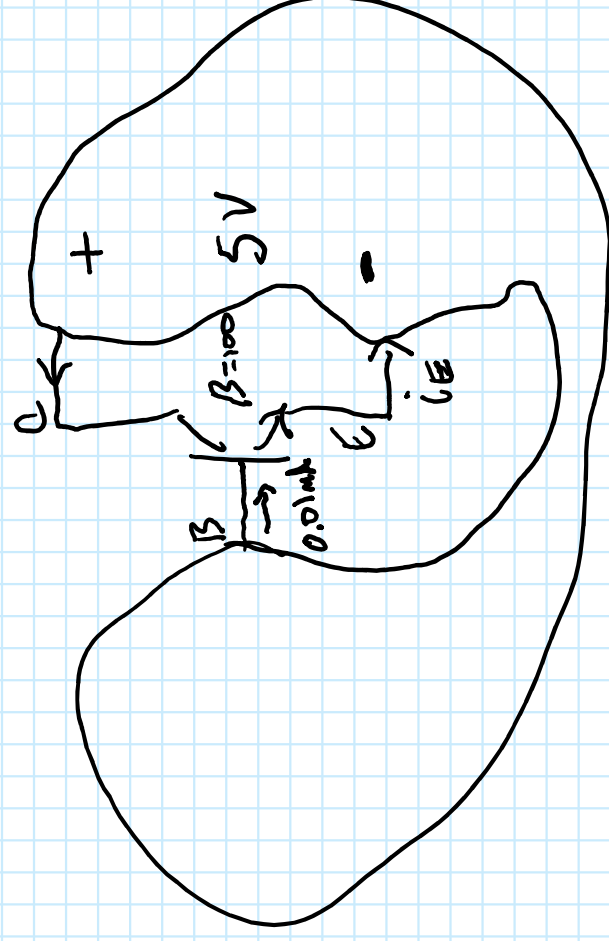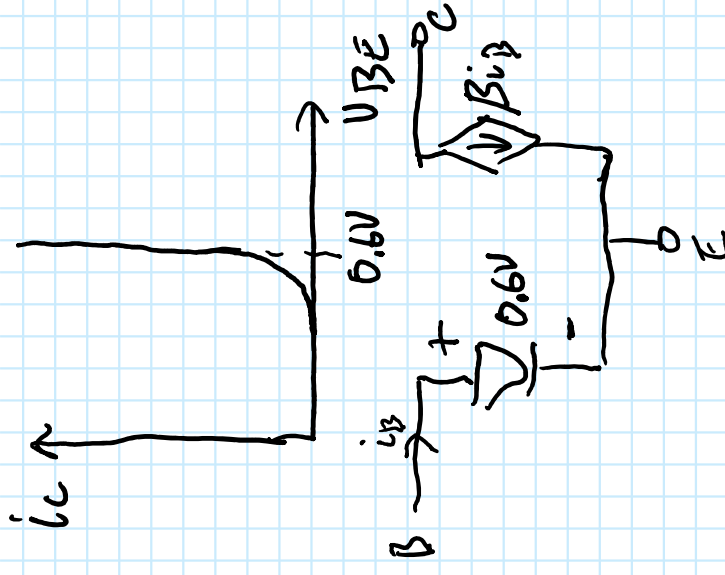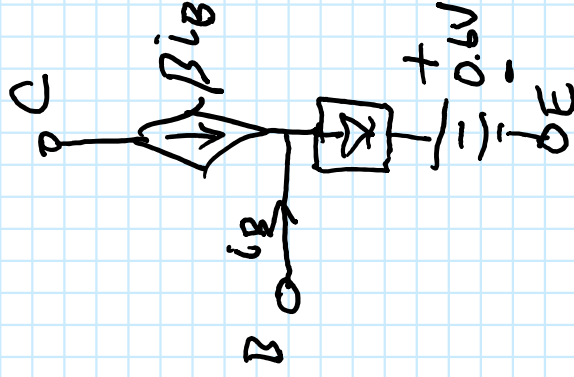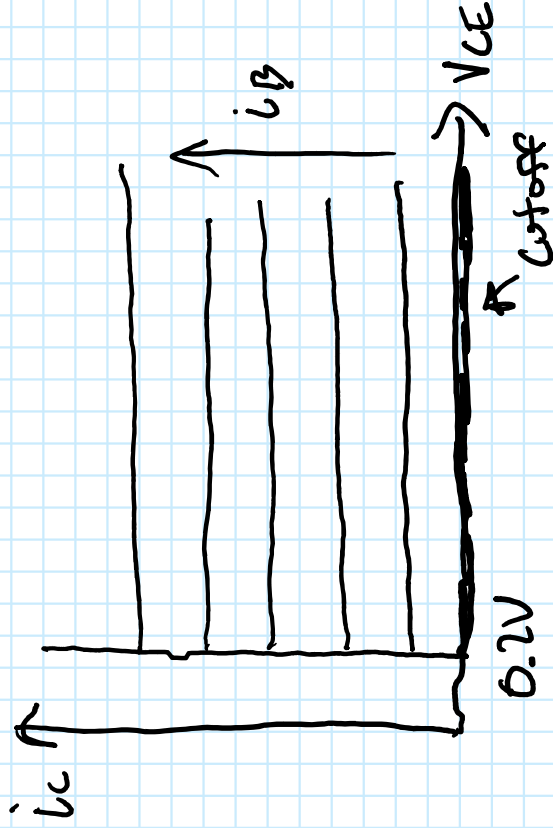

Find V_{BE}, i_c, i_e

① mode?

$$i_B > 0V$$

$$V_{CE} > 0.2V$$

$$i_c = \beta i_B = 1mA$$

$$i_e = (\beta + 1) i_B = 1.01mA$$

$$V_{BE} = 0.6V$$

COMMON EMITTER

AMP

V_{CC}

FIND V_{out} VS V_{in}

Assume Active Region

FIND V_{out} FOR $V_{in} = 1V, 1.1V, 1.2V$


$$R_B = 100k\Omega$$

$$R_C = 10k\Omega$$

$$\beta = 100$$

$$V_{CC} = 10V$$

$$V_{IN} = V_{DC} + V_{in}$$

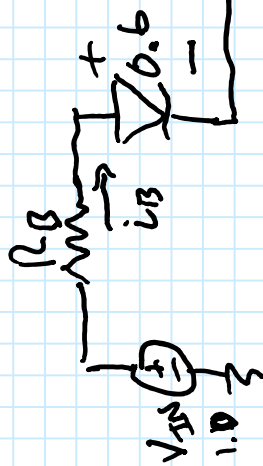

V_{IN}	V_{OUT}
1.0	6V
1.1	5V
1.2	4V

MOSFET V_{DD} - high
 V_{SS} - low

BJT V_{CC} - high
 V_{EE} - low

$$I_B = \frac{V_{IN} - 0.6}{R_B} = \frac{0.4V}{100k}$$

$$I_B = 4\mu A$$

$$I_C = 400\mu A = 0.4mA$$

$$I_E = 404\mu A$$

$$V_{out} = V_{CC} - I_C R_C$$

$$= 10 - 0.4mA(10k)$$

$$= 10 - 4 = 6V$$

$$V_{out} = V_{CC} - \beta I_B R_C = 10 - 100 \left(\frac{100k}{100k} \right) (V_{IN} - 0.6)$$

$$\frac{V_{CC} - V_{out}}{R_C} = I_C = \beta I_B$$

$$\frac{V_{CC} - V_{out}}{R_C} = \beta \frac{V_{IN} - 0.6}{R_B}$$

$$= 10 - 10V_{IN} + 6$$

$$= 16 - 10V_{IN}$$


COMMON EMITTER TRANSFER CHARACTERISTICS

LARGE-SIGNAL ANALYSIS

① TRANSFER CURVE $\rightarrow V_{out}$ vs V_{in}

② VARIOUS INPUT & OUTPUT OPERATING VOLTAGES
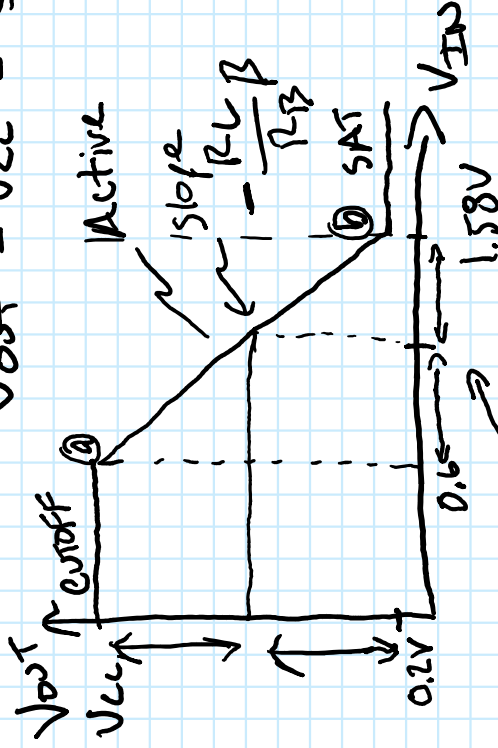
$$V_{out} = V_{cc} - \frac{(V_{in} - 0.6)}{R_B} R_L \beta$$



$$0.6V < V_{in} < 1.58V$$

CHOOSE OPERATING POINT

TO MAXIMIZE V_{in} SWING

\rightarrow Pick middle point of V_{in} range


\rightarrow linear transfer function means

output voltage also in middle of range

$$V_{CE} > 0.2V$$

$$V_{BE} = 0.6V$$

$$V_{CB} > -0.4V$$

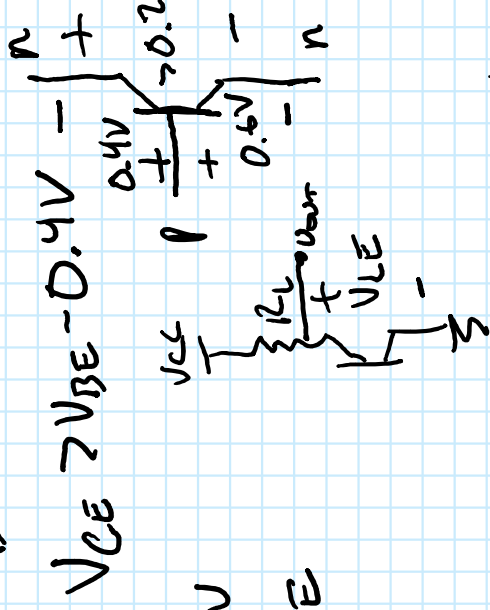

$$\textcircled{b} V_{CE} = 0.2V$$

$$V_{out} = V_{CE}$$

$$I_C \text{ at } \textcircled{b}$$


$$I_C = \frac{V_{CE} - V_{out}}{R_L}$$

$$= \frac{10 - 0.2}{10k} = 980\mu A = \beta I_B = \beta \left(\frac{V_{in} - 0.6}{R_B} \right)$$

$$V_{in} = 9.8\mu A \cdot R_B + 0.6$$

$$= 1.58V$$


CHAPTER 8: SMALL SIGNAL ANALYSIS

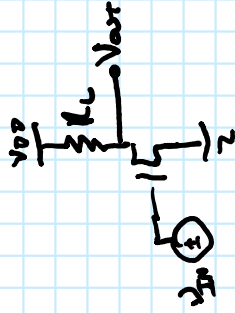

$$V_{out} = V_{DD} - i_D R_L$$

$$= V_{DD} - \frac{\mu}{2} (V_{IN} - V_T)^2 R_L$$

\Rightarrow Non-linear



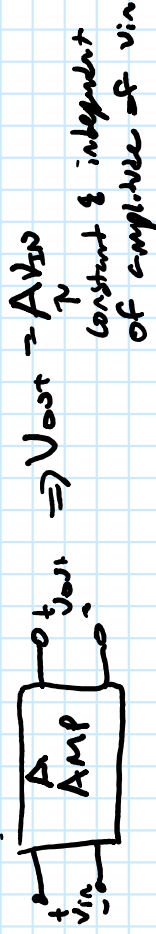


SMALL-SIGNAL


if signals can be represented as small perturbation about an operating point \rightarrow response of circuit will be approx. linear
 - linear model for a nonlinear device but only valid over small range
 LARGE-SIGNAL - valid over large range but complicated (nonlinear)

TOTAL VARIABLE DC Value S.S.

$$V_{IN} = V_{IN} + v_{in}$$

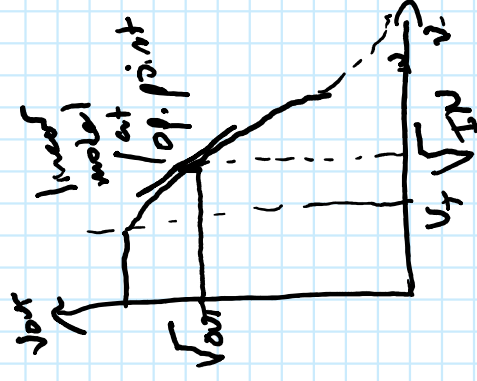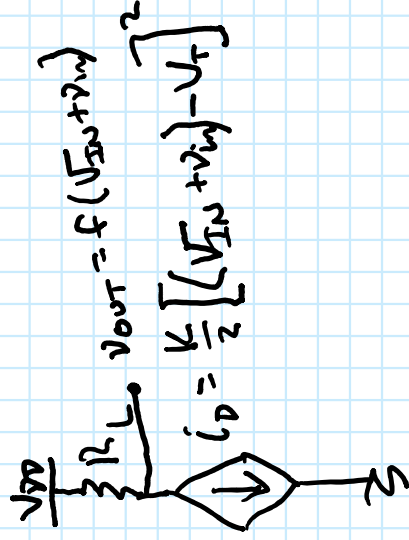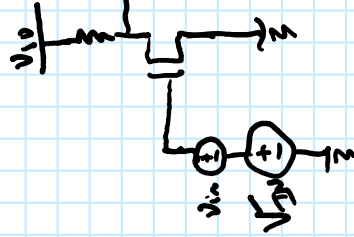

TAYLOR SERIES EXPANSION

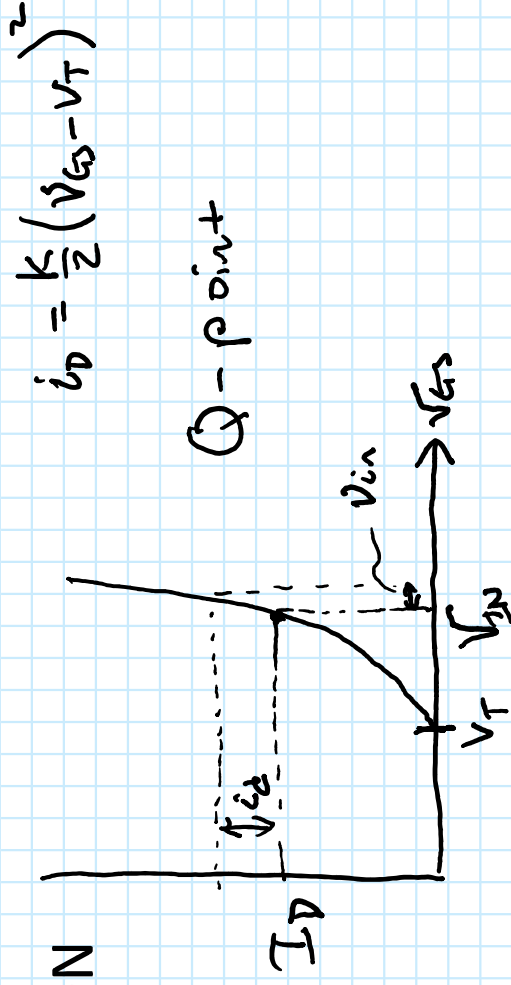

$$y = f(x) \text{ expand about } x = x_0$$

$$y = f(x_0) + \frac{df}{dx} \bigg|_{x_0} (x - x_0) + \frac{1}{2!} \frac{d^2f}{dx^2} \bigg|_{x_0} (x - x_0)^2 + \dots$$

$$y = i_D \quad V_{IN} = x_0 \quad x = V_{IN} + v_{in} \rightarrow x - x_0 = v_{in}$$

$$= I_D + i_d$$

$$i_D = \underbrace{\frac{K}{2} (V_{IN} - V_T)^2}_{\text{Exact}} + \underbrace{K(V_{IN} - V_T)v_{in} + \frac{K}{2} v_{in}^2}_{\text{linear approximation}}$$

v_{in} is small compared to V_{IN}

g_m = incremental transconductance

$$i_d = g_m v_{in}$$

$$g_m = K(V_{GS} - V_T)$$

OUTPUT AND GAIN

$$V_{out} = \underbrace{V_{out}}_{DC} + \underbrace{V_{out}}_{S.S.}$$

$$V_{out} = V_{DD} - i_D R_L$$


$$\begin{aligned} V_{out} + V_{out} &= V_{DD} - (I_D + i_d) R_L \\ &= \underbrace{V_{DD} - I_D R_L}_{V_{out, DC}} - \underbrace{i_d R_L}_{S.S.} \end{aligned}$$

$$i_d = g_m v_{in}$$


$$V_{out} = -i_d R_L = -g_m R_L v_{in}$$

S.S. GAIN
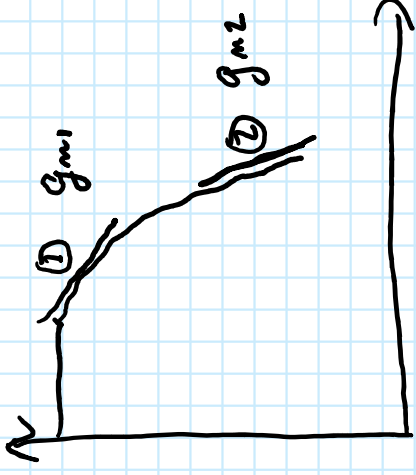
$$A = \frac{V_{out}}{v_{in}} = -g_m R_L = -\underbrace{g_m}_{\text{constant}} (\underbrace{V_{IN} - V_T}) R_L$$




SS EXAMPLE: DIODE CONNECTED MOSFET

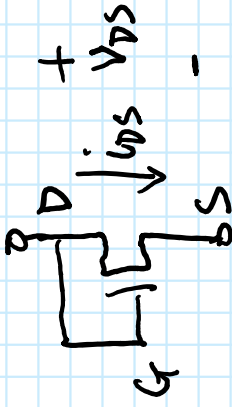

$$i_{DS} = K \frac{(V_{GS} - V_T)^2}{2}$$

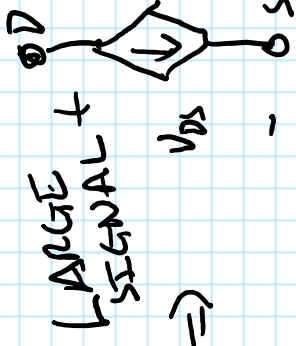
$$V_{GS} = V_{DS} \Rightarrow i_{DS} = \frac{K}{2} (V_{DS} - V_T)^2 \Rightarrow$$



$$i_{DS} = \frac{di_{DS}}{dV_{DS}} \bigg|_{V_{DS}}$$


$$= K (V_{DS} - V_T) \bigg|_{V_{DS}}$$
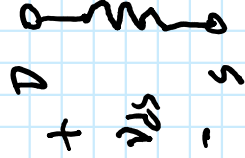
$$r_{DS} = \frac{i_{DS}}{K(V_{DS} - V_T)}$$




\Rightarrow Small signal acts like a resistor \rightarrow large resistance in small area
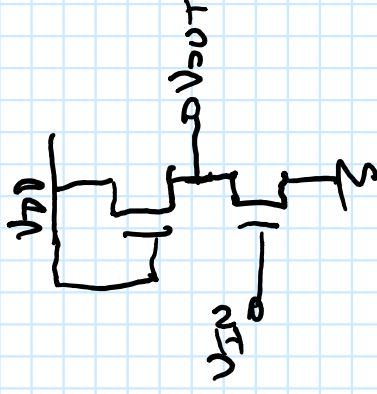
$$r = \frac{1}{K(V_{DS} - V_T)} = \frac{1}{g_m}$$








MODELS

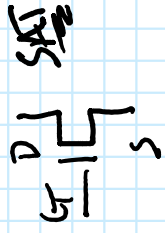

LARGE SIGNAL
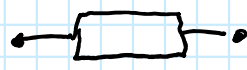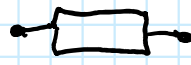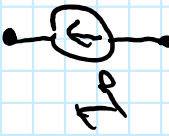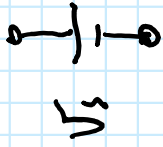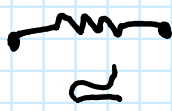
$$i_{DS} = K \frac{(V_{GS} - V_T)^2}{2}$$



SMALL SIGNAL


$$i_{ds} = K(V_{GS} - V_T)V_{DS} = g_m v_{gs}$$



AC
GROUND


$$i_a = \frac{df(v_A)}{dv_A} v_A$$

$$v_a = \frac{df(i_A)}{di_A} i_a$$

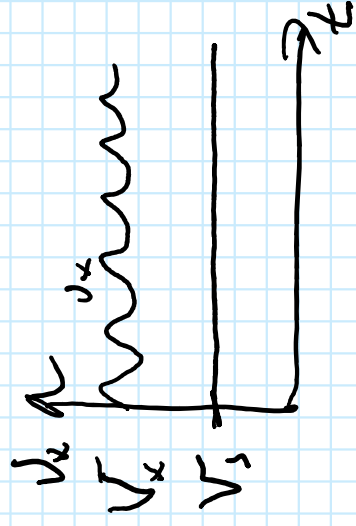


S.S. ANALYSIS OF COMMON SOURCE

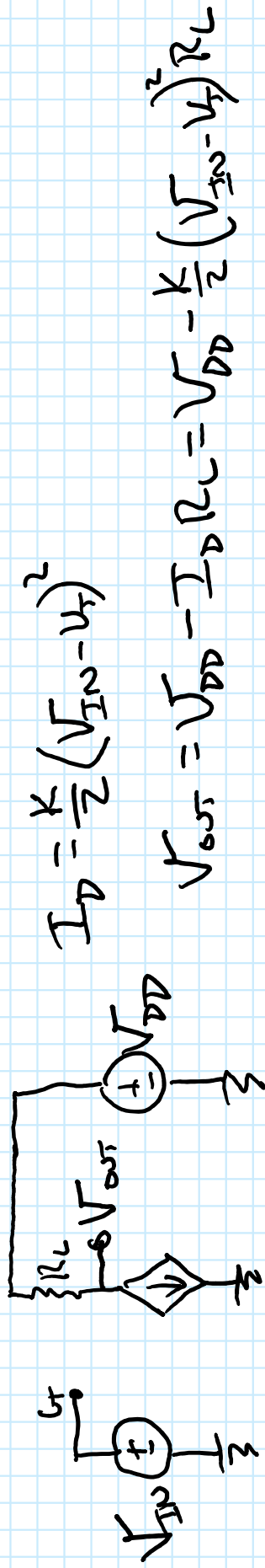AMP ① LARGE-SIGNAL ANALYSIS \Rightarrow DC Operating Point



② SS EQUIVALENT CIRCUIT

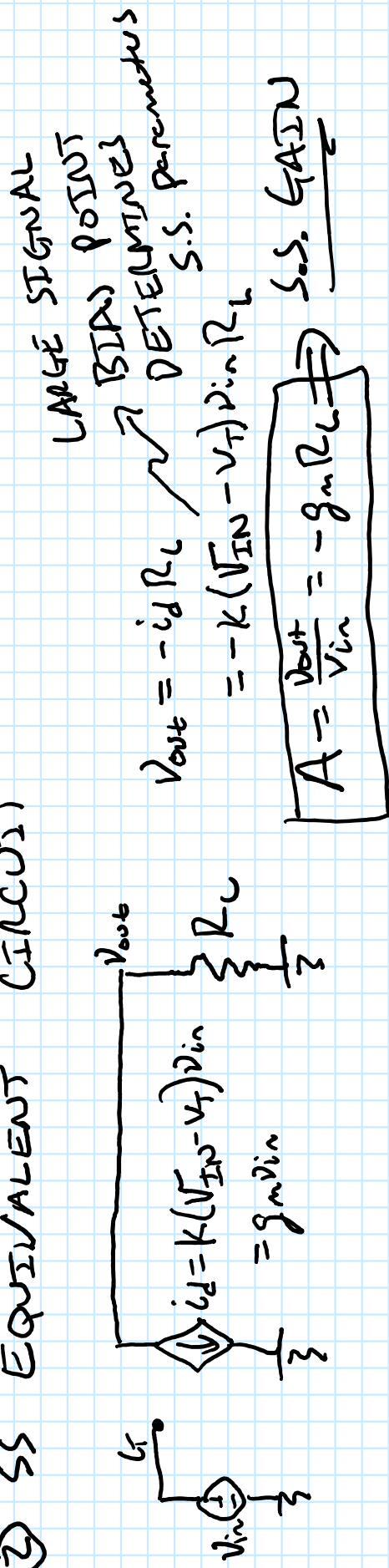

$$V_{DD} = 10V \quad K = 1mA/V^2$$

$$R_L = 10k\Omega \quad V_T = 1V$$

$$V_{IN} = 2V$$

$$V_{OUT} = 5V$$

What is A? $\frac{v_{out}}{v_{in}} = 10^3 (2-1)10^4 = 10$

What is V_{OUT}